Experiment #4-Integrated System

Narges Gholami, 810198447

1-Integrated System

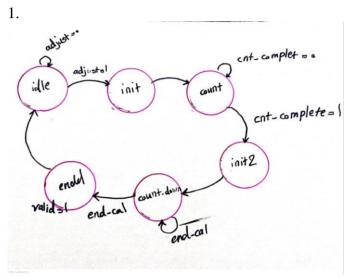


Fig1: state machine

2. testbench result in modelsim simulation software Input frequency = 100kHz



Fig2: n = 1 and frequency become 200 kHz

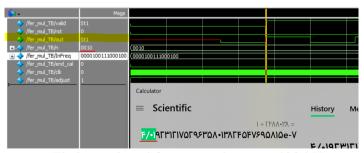



Fig3: n = 2 and frequency become 400 kHz



Fig 4: n = 3 and frequency become 800 kHz

2 Exponential Accelerator


2.1 Exponential Engine

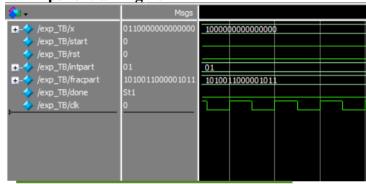

 $e^{0.5} = 1.6487212707001$



Fig5: input x = 0.5 and output is correct based on calculation

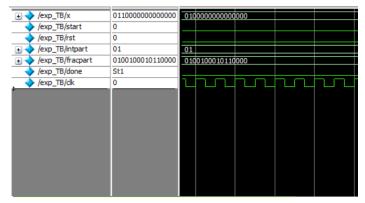

 $e^{0.25} = 1.2840254166877$


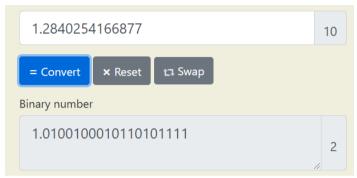


Fig6: input x = 0.25 and output is correct based on calculation

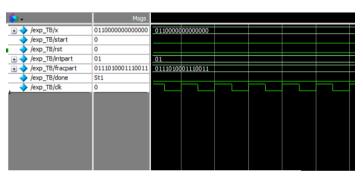

 $e^{0.375} = 1.4549914146182$



Fig6: input x = 0.375 and output is correct based on calculation



Fig7: synthesis summary

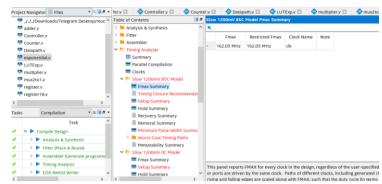


Fig8: maximum frequency of this accelerator is 162.5 MHz

2.2 Exponential Accelerator Wrapper

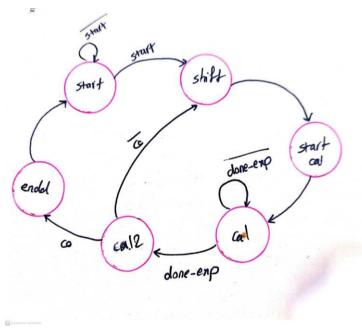


Fig9: state diagram of Wrapper

4- Assume x = 1.1

$e^{1.1} = 3.0041660239464$



$e^{1.2} = 3.3201169227365$



$e^{1.4} = 4.0551999668447$



 $e^{1.8} = 6.0496474644129$



Fig11: expected value for n = 4



Fig12: achieved results.

 $n = 0 \rightarrow answer = 2.2$ $n = 1 \rightarrow answer = 2.4$ $n = 2 \rightarrow answer = 2.9$ $n = 3 \rightarrow answer = 4.22$

It has difference with expected value because of approximation

Second example: x = 0.01

$e^{0.08} = 1.083287067675$



$e^{0.04} = 1.0408107741924$



$e^{0.02} = 1.0202013400268$



$e^{0.01} = 1.0100501670842$



Fig13: expected value for n = 4



Fig14: achieved results

```
n = 0 \rightarrow answer = 1.009

n = 1 \rightarrow answer = 1.02

n = 2 \rightarrow answer = 1.04

n = 3 \rightarrow answer = 1.08
```

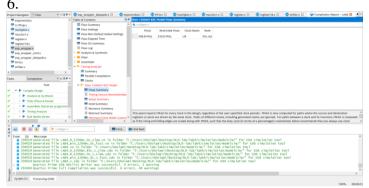


Fig15: Synthesis summary

 $\label{eq:maximum frequency of this accelerator wrapper is $250 MHz$$

3. Integrated Circuit

2- $162*10^6 / 200*10^3 = 810 \rightarrow [\log 810] = 9 \rightarrow \text{n needs 4 bit}$

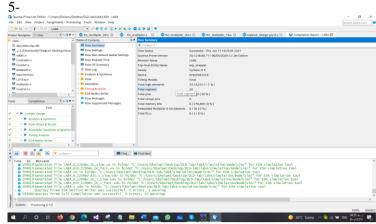


Fig16: Synthesis summary